

SULIT



BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI

JABATAN KEJURUTERAAN MEKANIKAL

PEPERIKSAAN AKHIR

SESI JUN 2016

DJJ2022: ELECTRICAL TECHNOLOGY

TARIKH : 03 NOVEMBER 2016
MASA : 2.30 PM - 4.30 PM (2 JAM)

Kertas ini mengandungi **TUJUH (7)** halaman bercetak.
Empat (4) soalan berstruktur
Dokumen sokongan yang disertakan : Kertas Graf, **Formula** dsb / Tiada

JANGAN BUKA KERTAS SOALAN INI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

INSTRUCTION:

This section consists of **FOUR (4)** essay questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi EMPAT (4) soalan esei. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**CLO1
C1

- (a) List **FOUR (4)** factors that influence the value of resistance
Senaraikan EMPAT (4) faktor yang mempengaruhi nilai rintangan

[4 marks]

[4 markah]

CLO1
C2

- (b) A bread maker with 5kW power, 230 voltage is used for baking 25 breads for half an hour. Calculate:

Pembakar Roti dengan kuasa 5kW, 230 voltan digunakan untuk membakar 25 roti selama setengah jam. Kira:

- i. Current (I)
Arus

[2 marks]

[2 markah]

- ii. Resistance (R)
Rintangan

[2 marks]

[2 markah]

- iii. Electrical energy if the circuit is being used for half an hour.
Tenaga elektrik jika litar digunakan selama setengah jam.

[2 marks]

[2 markah]

CLO1
C4

(c) Based on Figure 1(c), determine.
Berdasarkan Rajah 1(c), tentukan:

- Total resistance, R_T
Jumlah rintangan, R_T
- Total current, I_T
Jumlah arus, I_T
- Current flow through resistor 3Ω , I_2 and resistor 6Ω , I_3
Arus melalui perintang 3Ω , I_2 dan perintang 6Ω , I_3
- Voltage drop through resistor 2Ω
Voltan susut melalui perintang 2Ω

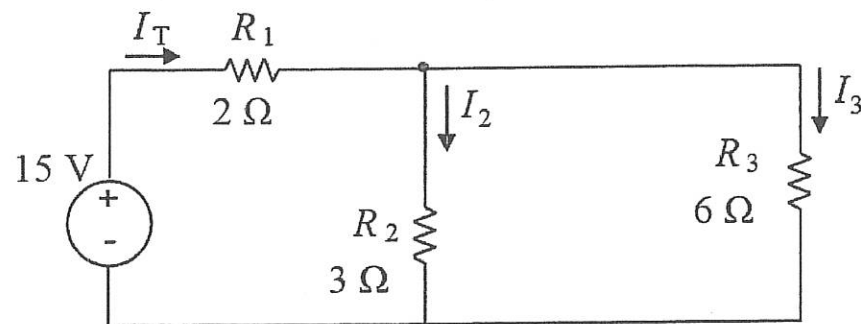


Figure 1(c) / Rajah 1(c)

[15 marks]

[15 markah]

QUESTION 2

SOALAN 2

CLO1
C1

- (a) State **THREE (3)** factors affecting the value of the capacitance of a capacitor in electrical circuit.

Nyatakan **TIGA (3)** faktor yang mempengaruhi nilai kemuatan pemuat dalam litar elektrik.

[5 marks]

[5 markah]

CLO1
C2

- (b) An Alternating current circuit has $50\angle 30^\circ\Omega$ impedance, assuming the frequency is 50Hz. Determine the AC circuit, whether it is RL or RC.

Sebuah litar arus ulangalik mempunyai galangan $50\angle 30^\circ\Omega$, dengan mengaggap frekuensi 50Hz. Tentukan litar AU tersebut samada ianya RC atau RL.

[5 marks]

[5 markah]

CLO1
C4

- (c) Series RLC circuit with 50Ω , 10mH and $200\mu\text{F}$. Supplied with AC 240 V with 50Hz frequency. Calculate:

Litar siri RLC dengan 50Ω , 10mH dan $200\mu\text{F}$. Dibekalkan dengan bekalan AU 240V dengan frekuensi 50Hz. Kirakan:

- Total Impedance
Jumlah galangan
- Total current in the circuit
Jumlah arus dalam litar
- Voltage drop at each components; V_R , V_L and V_C
Kejatuhan voltan pada setiap komponen; V_R , V_L and V_C

[15 marks]

[15 markah]

QUESTION 3

SOALAN 3

CLO1
C2

- (a) There are four factors that affect electromagnetic strength.

Terdapat empat faktor yang mempengaruhi kekuatan electromagnet.

- i. Explain
- FOUR (4)**
- factors which influence the electromagnetic strength.

Terangkan EMPAT (4) faktor yang mempengaruhi kekuatan elektromagnet.

[8 marks]

[8 markah]

- ii. A current of 500mA is passed through a 600 turn coil wound at a toroid of mean diameter 10cm. Calculate the magnetic field strength.

Arus 500mA mengalir melalui 600 lilitan gegelung yang dililit pada toroid yang mempunyai diameter 10cm. Kirakan kekuatan medan magnet.

[4 marks]

[4 markah]

- (b) A core of stainless steel of 50cm length and cross sectional area 4 cm
- ²
- is wound with 1000 turns of coil and 5A current flowing through it. The value of relative permeability is 1200, calculate:

Satu bar besi teras mempunyai panjang 50cm dan luas permukaan 4cm² dililit dengan 1000 lilitan pengalir dan arus sebanyak 5A melaluinya. Nilai ketelapan relatif adalah 1200, kira:

- i. Magneto motive force,
- F_m

Daya gerak magnet, F_m

[2 marks]

[2 markah]

- ii. Magnetic field strength,
- H

Kekuatan medan magnet, H

[2 marks]

[2 markah]

- iii. Absolute permeability,
- μ

Ketelapan sebenar, μ

[2 marks]

[2 markah]

- iv. Flux density,
- B

Ketumpatan Fluks, B

[2 marks]

[2 markah]

- v. The value of flux,
- Φ

Nilai fluks, Φ

[2 marks]

[2 markah]

- vi. Reluctance,
- S

Engganan, S

[3 marks]

[3 markah]

QUESTION 4

SOALAN 4

CLO1
C1

- (a) State
- TWO (2)**
- types of transformer losses.

Nyatakan DUA (2) jenis kehilangan dalam pengubah.

[5 marks]

[5 markah]

CLO1
C2

- (b) Differentiate between rotor and stator

Bezakan rotor dan stator

[5 marks]

[5 markah]

CLO1
C3

- (c) A single phase transformer with 400 kVA rating has a primary winding resistance of 0.5Ω and a secondary winding resistance of 0.001Ω . The iron loss is 2.5 kW and the primary and secondary voltages are 5 kV and 320 V respectively. If the power factor of the load is 0.85, calculate :

Sebuah pengubah fasa tunggal dengan kuasa ketara 400kVA mempunyai rintangan belitan primer 0.5Ω dan rintangan belitan sekunder 0.001Ω . Kehilangan teras besi yang dialami pengubah ialah 2.5 kW dan nilai voltan primer dan sekunder masing-masing adalah 5 kV and 320 V. Jika faktor kuasa pengubah ini adalah 0.85, tentukan nilai:

- i. The Primary current (I_p)
Arus primer (I_p)
- ii. The Secondary current (I_s)
Arus sekunder (I_s)
- iii. Power losses
Kehilangan kuasa
- iv. Output power
Kuasa keluaran
- v. Input power
Kuasa masukan
- vi. The efficiency of the transformer when the transformer is on a full load stage.
Kecekapan pengubah jika pengubah berada dalam keadaan beban penuh.

[15 marks]

[15 markah]

SOALAN TAMAT



<p>INTRODUCTION TO ELECTRICAL CIRCUITS</p> $R = \frac{\rho l}{A} \quad V = IR$ $P = IV \quad E = Pt$ $C = \frac{Q}{V}$ <p>KIRCHOFF'S LAW $V_j = V_1 + V_2 + V_3$ $\Sigma I_{IN} = \Sigma I_{OUT}$ $I_1 = I_2 + I_3$</p> <p>SERIES</p> <table border="1"> <tr><td>$V_T = V_1 + V_2 + \dots + V_n$</td></tr> <tr><td>$I_T = I_1 = I_2 = \dots = I_n$</td></tr> <tr><td>$R_T = R_1 + R_2 + \dots + R_n$</td></tr> <tr><td>$L_T = L_1 + L_2 + \dots + L_n$</td></tr> <tr><td>$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$</td></tr> </table> <p>PARALLEL</p> <table border="1"> <tr><td>$V_T = V_1 = V_2 = \dots = V_n$</td></tr> <tr><td>$I_T = I_1 + I_2 + \dots + I_n$</td></tr> <tr><td>$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$</td></tr> <tr><td>$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$</td></tr> <tr><td>$C_T = C_1 + C_2 + \dots + C_n$</td></tr> </table>	$V_T = V_1 + V_2 + \dots + V_n$	$I_T = I_1 = I_2 = \dots = I_n$	$R_T = R_1 + R_2 + \dots + R_n$	$L_T = L_1 + L_2 + \dots + L_n$	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$	$V_T = V_1 = V_2 = \dots = V_n$	$I_T = I_1 + I_2 + \dots + I_n$	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$	$C_T = C_1 + C_2 + \dots + C_n$	<p>ALTERNATING CURRENT CIRCUIT</p> <table border="1"> <tr><td>RL CIRCUIT</td></tr> <tr><td>$I = \frac{V}{Z}$</td></tr> <tr><td>$V_L = IX_L$</td></tr> <tr><td>$Z = \sqrt{R^2 + X_L^2}$</td></tr> <tr><td>$\theta = \tan^{-1} \left[\frac{X_L}{R} \right]$</td></tr> <tr><td>$\cos \theta = \frac{R}{Z}$</td></tr> </table> <table border="1"> <tr><td>RC CIRCUIT</td></tr> <tr><td>$I = \frac{V}{Z}$</td></tr> <tr><td>$V_C = IX_C$</td></tr> <tr><td>$Z = \sqrt{R^2 + X_C^2}$</td></tr> <tr><td>$\theta = \tan^{-1} \left[\frac{X_C}{R} \right]$</td></tr> <tr><td>$\cos \theta = \frac{R}{Z}$</td></tr> </table> <table border="1"> <tr><td>RLC CIRCUIT</td></tr> <tr><td>$I = \frac{V}{Z}$</td></tr> <tr><td>$V_L = IX_L \quad V_R = IR$</td></tr> <tr><td>$V_C = IX_C$</td></tr> <tr><td>$Z = \sqrt{R^2 + (X_L - X_C)^2}$</td></tr> <tr><td>$\theta = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$</td></tr> <tr><td>$\cos \theta = \frac{R}{Z}$</td></tr> </table>	RL CIRCUIT	$I = \frac{V}{Z}$	$V_L = IX_L$	$Z = \sqrt{R^2 + X_L^2}$	$\theta = \tan^{-1} \left[\frac{X_L}{R} \right]$	$\cos \theta = \frac{R}{Z}$	RC CIRCUIT	$I = \frac{V}{Z}$	$V_C = IX_C$	$Z = \sqrt{R^2 + X_C^2}$	$\theta = \tan^{-1} \left[\frac{X_C}{R} \right]$	$\cos \theta = \frac{R}{Z}$	RLC CIRCUIT	$I = \frac{V}{Z}$	$V_L = IX_L \quad V_R = IR$	$V_C = IX_C$	$Z = \sqrt{R^2 + (X_L - X_C)^2}$	$\theta = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$	$\cos \theta = \frac{R}{Z}$	<p>AC MACHINES</p> $N_s = \frac{120f}{P} \quad \%S = \frac{N_s - N_r}{N_s} \times 100$ $N_r = N_s(1 - S) \quad f_r = Sf$ <p>TRANSFORMER</p> $\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p} \quad E_1 = 4.44 f N_1 \Phi_m$ $E_2 = 4.44 f N_2 \Phi_m$ <p>Complex Power, S (VA) = $\sqrt{3} V_L I_L$ Actual Power, P (W) = $\sqrt{3} V_L I_L \cos \theta$ Reactive Power, Q (VAR) = $\sqrt{3} V_L I_L \sin \theta$</p> <p>I = $\frac{\text{Power}}{\text{Voltage}}$</p> <p>Power losses = Core losses + $I_p^2 R_p$ + $I_s^2 R_s$ Output power = Power x power factor Input power = output power + power losses Efficiency, %$\eta = \frac{\text{output power}}{\text{Input power}} \times 100$</p> <p>ELECTROMAGNET</p> $H = \frac{Fm}{l} = \frac{NI}{l}$ $B = \frac{\Phi}{A}$ $B = \mu H$ $\mu = \mu_o \mu_r$ $S = \frac{Fm}{\Phi} @ \frac{l}{\mu A}$
$V_T = V_1 + V_2 + \dots + V_n$																															
$I_T = I_1 = I_2 = \dots = I_n$																															
$R_T = R_1 + R_2 + \dots + R_n$																															
$L_T = L_1 + L_2 + \dots + L_n$																															
$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$																															
$V_T = V_1 = V_2 = \dots = V_n$																															
$I_T = I_1 + I_2 + \dots + I_n$																															
$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$																															
$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$																															
$C_T = C_1 + C_2 + \dots + C_n$																															
RL CIRCUIT																															
$I = \frac{V}{Z}$																															
$V_L = IX_L$																															
$Z = \sqrt{R^2 + X_L^2}$																															
$\theta = \tan^{-1} \left[\frac{X_L}{R} \right]$																															
$\cos \theta = \frac{R}{Z}$																															
RC CIRCUIT																															
$I = \frac{V}{Z}$																															
$V_C = IX_C$																															
$Z = \sqrt{R^2 + X_C^2}$																															
$\theta = \tan^{-1} \left[\frac{X_C}{R} \right]$																															
$\cos \theta = \frac{R}{Z}$																															
RLC CIRCUIT																															
$I = \frac{V}{Z}$																															
$V_L = IX_L \quad V_R = IR$																															
$V_C = IX_C$																															
$Z = \sqrt{R^2 + (X_L - X_C)^2}$																															
$\theta = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$																															
$\cos \theta = \frac{R}{Z}$																															